

Hands on with FPGA's: Module 3

Venkat Rangan

Topics

- Pre-class: Open floor for questions
- Clocks:
 - What is a clock?
 - Why do we need a clock?
 - Interesting things about clocks
 - How are clocks used?
- Reset
 - What is a reset
 - Why do we need a Reset?
 - Variety of Reset's
- Intro to Verilog/Simulations/Synthesis
- Open discussion

Clocks in Digital Logic circuits

GAMING ENTERTAINMENT TECH

Intel's unlocked Core i9-12900KS processor claims to be the 'world's fastest desktop processor' with 5.5GHz speeds

But with a \$739 price tag, that speed won't come cheap

By Chaim Gartenberg | @cgartenberg | Mar 28, 2022, 12:52pm EDT


- What's the meaning of it all?
- Synchronous vs. Asynchronous design

How to Overclock Any Raspberry Pi

By Les Pounder published August 03, 2020

Turn up the clock speed on your Raspberry Pi.

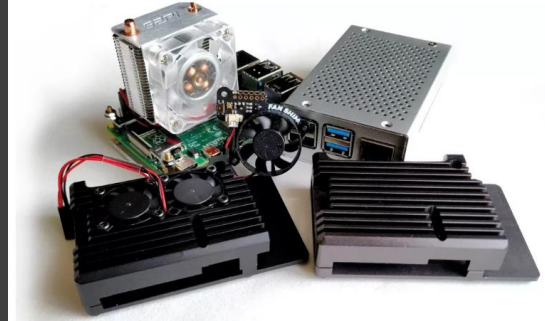
[f](#) [t](#) [v](#) [p](#) [y](#) [m](#) [c](#) Comments (11)



A selection of active and passive cooling products for the Raspberry Pi 4. (Image credit: Tom's Hardware)


Why clock?

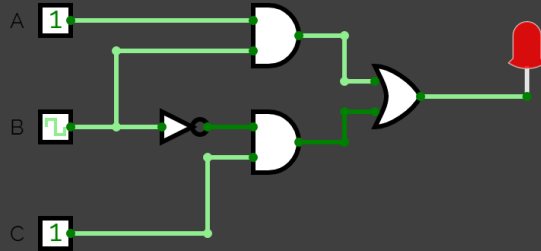- Clocks are one way for circuits to have memory
 - [SR Latch & D Flip Flop \(DFF\) in Circuitverse](#)
 - DFF forms the basis of most digital logic
- Digital Heartbeat
 - Synchronization between different parts of a design
 - Every circuit knows when its time to do something
- Glitches



Important properties of a Clock

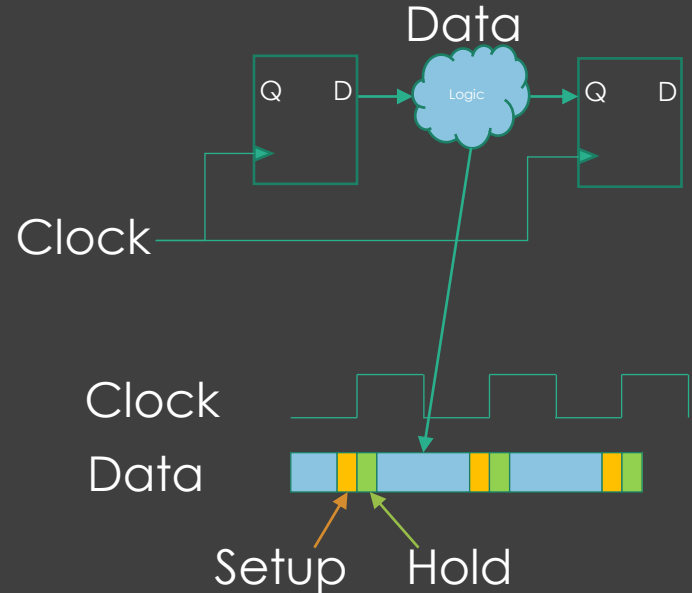- Frequency
- Duty Cycle
- Jitter
- Setup and Hold
- Max frequency of operation



Clocks in Verilog

- How does HW actually work?
 - Everything is running in parallel
 - All changes happen on the positive edge of a clock
 - Less commonly also on negative edge or both edges (DDR DRAM)
 - Between clock edges, signals propagate between registers

Clock Sources

- RC Oscillator
- Quartz Oscillator
- Exotic Sources
 - Temperature compensated, Oven Controlled
 - GPS/Atomic Clocks

Clocks: Good design practice

- Minimize number of clocks in your design
- Have a single clock unless absolutely necessary
- **Poor design** vs. **Good design** practice

```
// simple ripple clock divider
```

```
always @(posedge clk)
    clk_div2 <= ~clk_div2;
```

```
always @(posedge clk_div2)
    clk_div4 <= ~clk_div4;
```

```
always @(posedge clk_div4)
    clk_div8 <= ~clk_div8;
```

```
always @(posedge clk_div8)
    clk_div16 <= ~clk_div16;
```

```
// simple ripple clock divider
```

```
always @(posedge clk)
    clk_div2 <= reset ? 0 : ~clk_div2;
```

```
always @(posedge clk)
    if (clk_div2)
        clk_div4 <= ~clk_div4;
```

```
always @(posedge clk)
    if (clk_div4 & clk_div2) clk_div8 <= ~clk_div8;
```

```
always @(posedge clk)
    if ( &{clk_div2, clk_div4, clk_div8}) clk_div16 <= ~clk_div16;
```


Reset

- What state does a system start in?
 - Whats the state of wires at power up?
- “x”, “0”, “1” states
- Define using an external “Reset”

Verilog Deep Dive

- Pages 3-17 of [This presentation](#)

Module 3: Clocks and Verilog basics

Open Discussion