

# Hands on with FPGA's: Module 4

Venkat Rangan

# Topics

- Pre-class: Open floor for questions
  - Module 3 solutions
- Waveforms
- State Machines:
  - What is a State Machine?
  - Why do we need a State Machine?
- Verilog State Machines
- Brief overview of upcoming tasks
- Open discussion

# Review of Module 3


- Counter problem ([Solution](#))
- Oscillator Questions

## RP2040 Datasheet Excerpt

### 2.15.2.4. Relaxation Oscillators

If the user wants to use external clocks to replace or supplement the other clock sources but does not have an appropriate clock available, then 1 or 2 relaxation oscillators can be constructed using external passive components. Simply send the clock source (GPIN0 or GPIN1) to one of the gpclk0-3 generators, invert it through the GPIO inverter **OUTOVER** and connect back to the clock source input via an RC circuit.

Figure 29. Simple relaxation oscillator example

 


# Documentation: Waveforms

- Digital circuits are documented using waveforms
- Can show interaction of multiple blocks
- Good tool to learn: [Wavedrom](#)
  - Text based, open source

The following source code describes a DDR DRAM access:

```
{ signal: [  
  { name: "CK", wave: "P.....", period: 2 },  
  { name: "CMD", wave: "x.3x=x4x=x=x=x",  
    data: "RAS NOP CAS NOP NOP NOP", phase: 0.5 },  
  { name: "ADDR", wave: "x.=x.=x.....",  
    data: "ROW COL", phase: 0.5 },  
  { name: "DQS", wave: "z.....0.1010z." },  
  { name: "DQ", wave: "z.....5555z.",  
    data: "D0 D1 D2 D3" }  
]}
```


Below is the rendered waveform.

 

# State Machines: Practical uses


- RP2040 PIO peripheral

Figure 38. PIO block-level diagram. There are two PIO blocks with four state machines each. The four state machines simultaneously execute programs from a shared instruction memory. FIFO data queues buffer data transferred between PIO and the system. GPIO mapping logic allows each state machine to observe and manipulate up to 30 GPIOs.

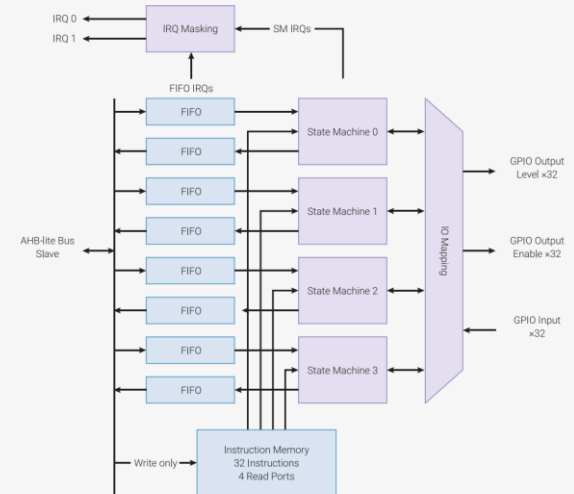

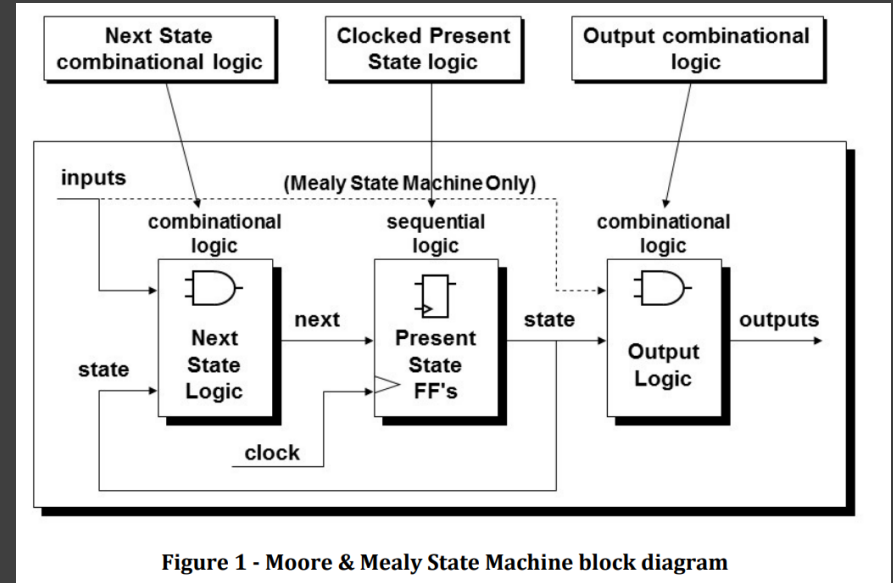
# State Machines

- [SunBurst Design Paper](#)
- Moore vs Mealy
  - Mealy outputs depend on inputs
  - Moore outputs only depend on current state
- Do not use Mealy unless necessary
  - Usually lowers max clock rate



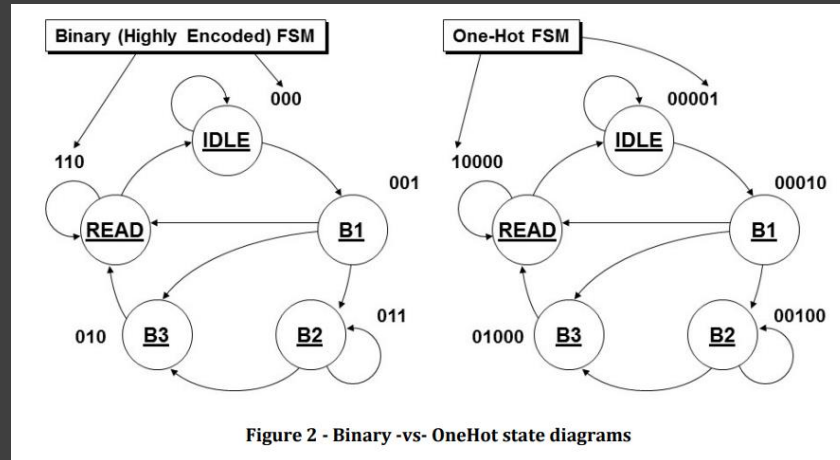
# State Encoding

- One-hot vs. Binary vs. others
  - Preference: One-hot for FPGA's, Binary for ASIC
  - Other encoding schemes for error resistance/tolerance. E.g. space, military



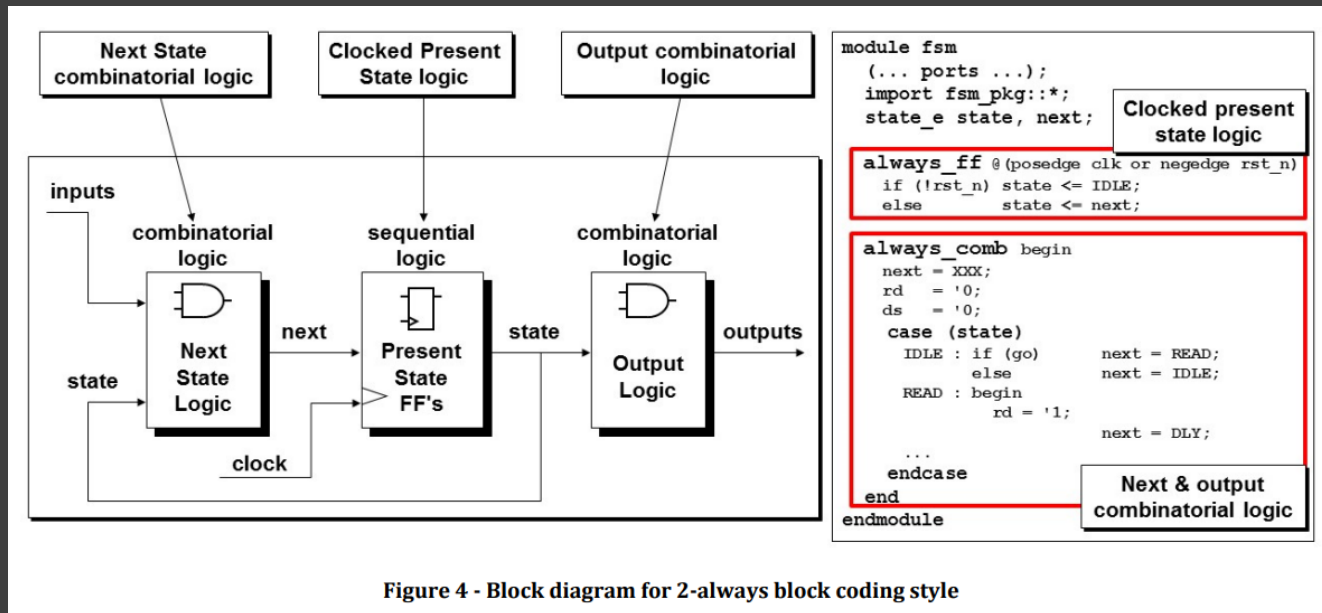
# Verilog Coding Style for FSM's: 2 always blocks






# Verilog Coding Style for FSM's: 3 always blocks

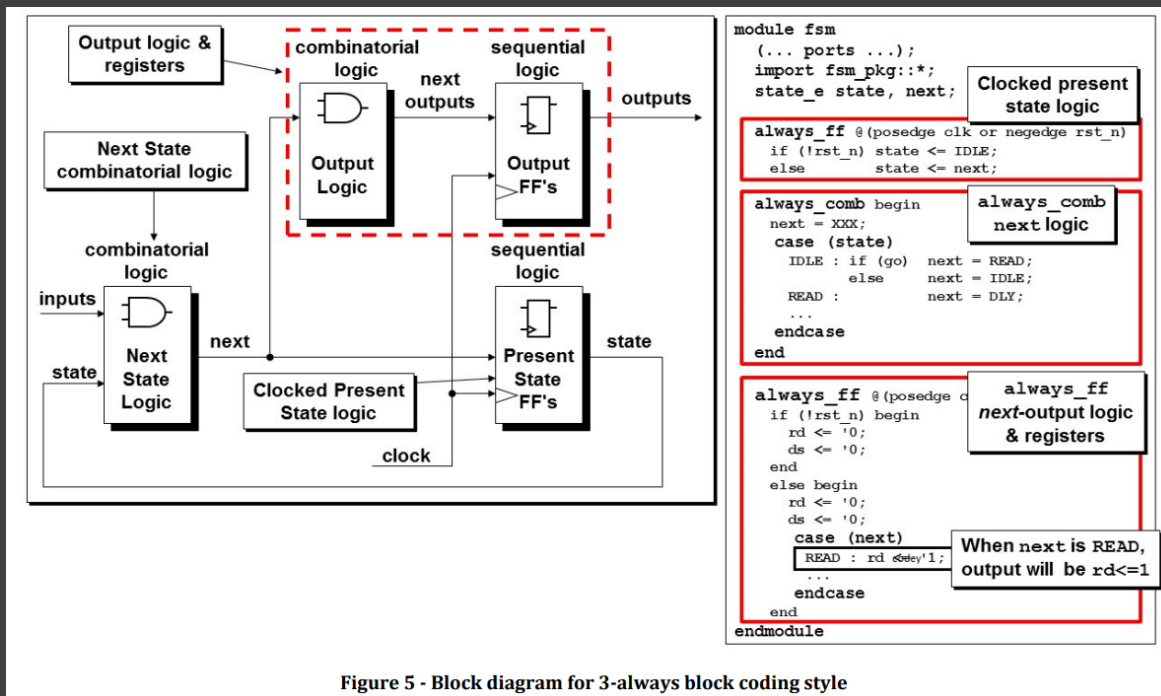

**Figure 5 - Block diagram for 3-always block coding style**
 
# Verilog Deep Dive

- EDA Playground
  - Default FSM Example
    - No reset!
    - Poor readability, tough to debug
  - “Fixed” FSM Example
    - Added reset
    - Much more readable
    - Trap state for unknowns
- GTKWave
  - Open source waveform viewer
  - Critical tool for HW debug during simulations



# Module 4: State Machines

- Tasks
  - Read the Sunburst design paper on state machines
  - Understand the various coding styles
  - Try it out!
- Challenge
  - Code up a state machine for a traffic light

# Open Discussion